

THE HONG KONG POLYTECHNIC UNIVERSITY  
HONG KONG COMMUNITY COLLEGE

**Subject Title** : Introduction to Electrical Systems      **Subject Code** : CCN2270

**Session** : Semester One, 2017/18

**Numerical Answers**

**Question A1**

- (a)  $P_{in} = 40 \text{ kW}$  and  $Q_{in} = 30 \text{ kVAR}$   
(b)  $S_c = -j12.96 \text{ kVA}$

**Question A2**

$\eta = 96.44\%$

**Question A3**

$R_1 = 0.116 \Omega, R_2 = 0.083 \Omega, X_1 = X_2 = j0.0735 \Omega, X_M = j6.5325 \Omega$

**Question A5**

- (a)  $\text{GMR} = 0.0218 \text{ m}$   
(b)  $A = D = 1, C = 0, B = j15.058 \Omega$

**Question A6**

Speed = 2947 rpm  
Current = 27.8 A

**Question B1**

- (a)  $R_{c,pu} = 103.306 \text{ pu}, X_{M,pu} = j21.087 \text{ pu}, Z_{eq,pu} = 0.0413 + j0.2025 \text{ pu}$

**Question B2**

$X_{s,G1} = j0.16 \text{ pu}, X_{s,G2} = j0.125 \text{ pu}, X_{s,T1} = j0.4 \text{ pu}, X_{s,T2} = j0.3 \text{ pu}$   
 $Z_{L1} = 0.265 + j0.661 \text{ pu}, Z_{L2} = 0.529 + j0.926 \text{ pu}, Z_{L1} = -j0.132 \text{ pu}$   
 $Z_{load} = 4.444 \angle 31.79^\circ \text{ pu}$

**Question B3**

- (a)  $S_A = 65.619 \text{ MVA} \angle -35.29^\circ, S_B = 34.454 \text{ MVA} \angle -39.88^\circ$   
(b)(i)  $I_{rated,in} = 25 \text{ A}, I_{rated,out} = 22.727 \text{ A}$

(b)(ii)  $S_w = 2.727 \text{ kVA}$

**Question B4**

- (a)  $E_A = 7580.211 \angle 12.8^\circ \text{ V}$
- (b) V. R. = 19.36%,  $\eta = 62.75\%$
- (c)  $V_T = 13.129 \text{ kV}$
- (d)  $Q_{3\phi} = 1.233 \text{ MVAR}$ ,  $P_{3\phi} = 800 \text{ kW}$