

THE HONG KONG POLYTECHNIC UNIVERSITY
HONG KONG COMMUNITY COLLEGE

Subject Title : Introduction to Electrical Systems **Subject Code** : CCN2270

Session : Semester One, 2018/19

Numerical Answers

Question A1

$$R_C = 12.5 \text{ pu}, X_M = j0.5834 \text{ pu}, Z_{eq} = 0.537 \angle 85.478^\circ \text{ pu}$$

Question A2

- (a) $n_m = 1500 \text{ rpm}$
- (b) $P_{CU} = 1.636 \text{ kW}$

Question A3

$$\text{V.R.} = 2.15\%, \eta = 88.48\%$$

Question A4

- (a) $X_S = j0.2 \text{ pu}, X_{eq} = j0.05 \text{ pu}, Z_{line} = 1.653 + j4.959 \text{ pu}, Z_{load 1} = 826.45 \text{ pu}$
 $Z_{load 2} = 8.26 \angle 45^\circ \text{ pu}$
- (c) $I_G = 0.0756 \angle -55.13^\circ \text{ pu}$

Question A5

$$n_1 = 4246 \text{ rpm}$$

Question A7

- (a) $\text{GMR} = 0.021 \text{ m}$
- (b) $X_L = 2.843 \times 10^{-4} \Omega/\text{m}$

Question B1

- (a) $X_M = j172.063 \Omega, X_1 = X_2 = j10.765 \Omega, R_2 = 6.73 \Omega, R_1 = 12.5 \Omega$
- (b) 306 W
- (c) 40.72 W

Question B2

- (b) PF = 0.85, lagging
- (c) $P_{3\phi} = -28.114 \text{ kW}$, $Q_{3\phi} = -17.389 \text{ kVAR}$
- (d) $I_{A, new} = 17.964 \angle -18.58^\circ \text{ A}$

Question B4

- (a) $S_{Total} = 157 - j5.566 \text{ MVA}$
- (c) $PF_1 = 0.3924$, lagging, $PF_2 = 0.3825$, leading