

THE HONG KONG POLYTECHNIC UNIVERSITY
HONG KONG COMMUNITY COLLEGE

Subject Title : Aircraft Electricity and Electronics **Subject Code** : CCN2288

Session : Semester Two, 2017/18

Numerical Answers

Question A1

$$V_1 = 3.2 \text{ V}$$

Question A2

(a) $I_s = 2.39 \angle 1.47$ or $2.39 \angle 84.3^\circ \text{ A}$

(b) $I_1 = 2.39 \angle -1.67$ or $2.39 \angle -95.7^\circ \text{ A}$, $I_2 = 4.78 \angle 1.47$ or $4.78 \angle 84.3^\circ \text{ A}$

Question A3

(a) 4

(b) $I_p(t) = 0.5 \cos(2\pi \times 50t) \text{ A}$

Question A4

(a) $1000 \ 1001_2$

Question A5

(b)(ii) $\tilde{I}_a = 30 - j30$ or $42.4 \angle -0.785$ or $42.4 \angle -45^\circ \text{ A}$

$$\tilde{I}_b = -41.0 - j11.0 \text{ or } 42.4 \angle -2.88 \text{ or } 42.4 \angle -165^\circ \text{ A}$$

$$\tilde{I}_c = 11.0 - j41.0 \text{ or } 42.4 \angle 1.31 \text{ or } 42.4 \angle 75^\circ \text{ A}$$

Question B1

(b)(i) 0.847

(b)(ii) $S = 94.8 + j59.6$ or $112 \angle 0.561$ or $112 \angle 32.1^\circ \text{ VA}$

(b)(iii) $P = 94.8 \text{ W}$, $Q = 59.6 \text{ VAR}$

(b)(iv) $C = 14.3 \ \mu\text{F}$

Question B2

(c)(ii) $V_{\text{amp}} = 8.53 \text{ V}$

(d)(iii) $R = 406 \ \Omega$

Question B3

- (a)(i) $R_{z, \max} = 365 \Omega$
- (a)(ii) $P = 54 \text{ mW}$
- (a)(iv) $R = 23.5 \text{ k}\Omega$
- (b)(ii) $I_C = 176 \text{ mA}$, $V_{CE} = 18.0 \text{ V}$, $P = 0.310 \text{ W}$
- (b)(iii) $I_C = 0.488 \text{ A}$, $R_{B1} = 88.2 \Omega$